

# What Does Stability Mean?

- Stability circles determine what load or source impedances should be avoided for stable or non-oscillatory amplifier behavior
- Because reactive loads are being added to amp the conditions for oscillation must be determined
- So the Output Stability Circle determine the  $\Gamma_L$  or load impedance (looking into matching network from output of amp) that may cause oscillation
- Input Stability Circle determine the  $\Gamma_S$  or impedance (looking into matching network from input of amp) that may cause oscillation

## Criteria for Unconditional Stability

- Unconditional Stability when amplifier remains stable throughout the entire domain of the Smith Chart at the operating bias and frequency. Applies to input and output ports.
- For  $|S_{11}| < 1$  and  $|S_{22}| < 1$ , the stability circles reside completely outside the  $|\Gamma_S| = 1$  and  $|\Gamma_L| = 1$  circles.

# Unconditional Stability: Rollett Factor

- $|C_{in}| - r_{in} | > 1$  and  $|C_{out}| - r_{out} | > 1$
- Stability or Rollett factor  $k$ :

$$k = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}||S_{21}|} > 1$$

with  $|S_{11}| < 1$  or  $|S_{22}| < 1$


and

$$|\Delta| = |S_{11}S_{22} - S_{12}S_{21}| < 1$$


## Stabilization Methods

- Stabilization methods can be used to for operation of BJT or FET found to be unstable at operating bias and frequency
- One method is to add series or shunt conductance to the input or output of the active device in the RF signal path to “move” the source or load impedances out of the unstable regions as defined by the Stability Circles
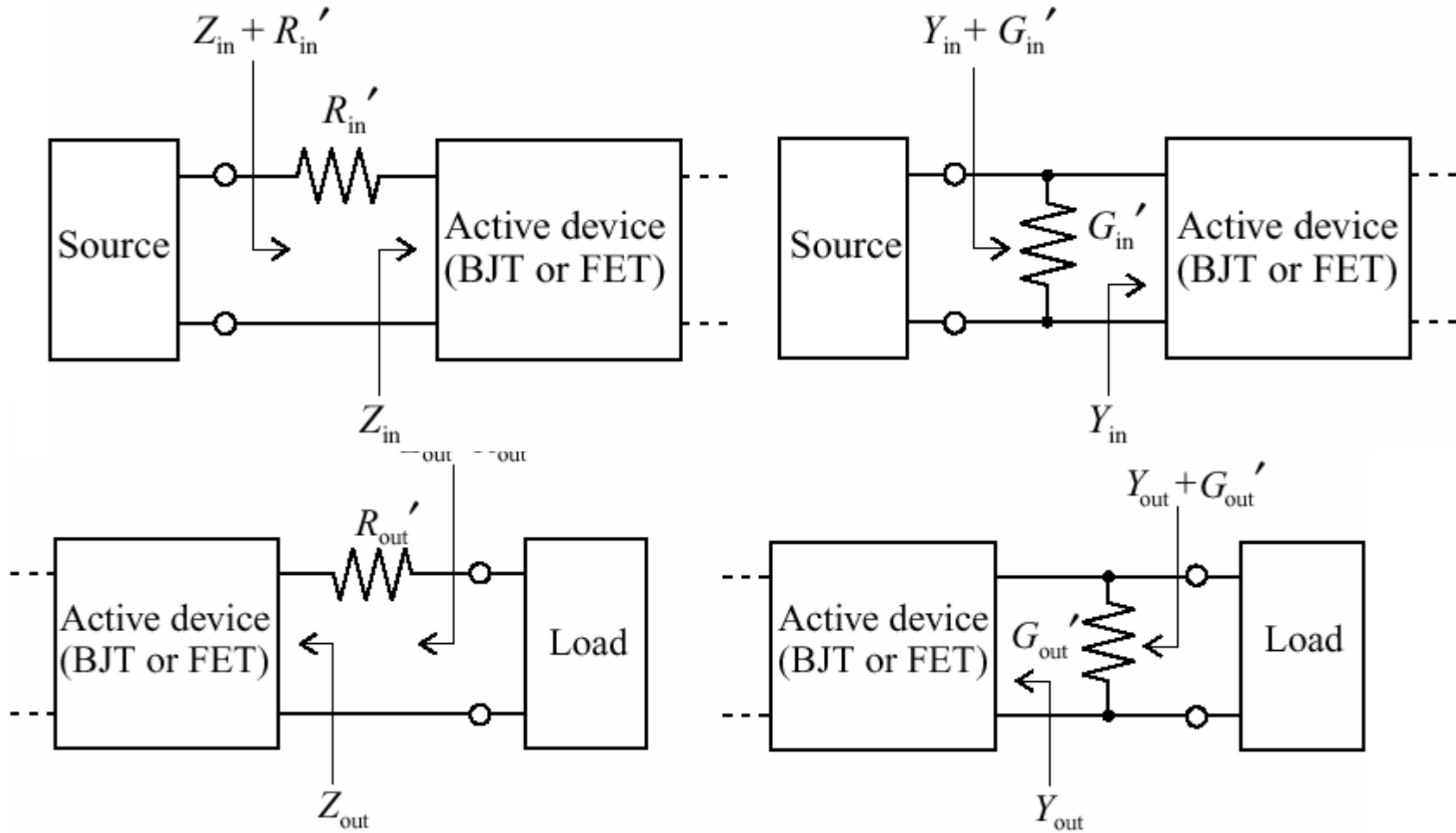
# Stabilization Using Series Resistance or Shunt Conductance




# Stabilization Method: Smith Chart

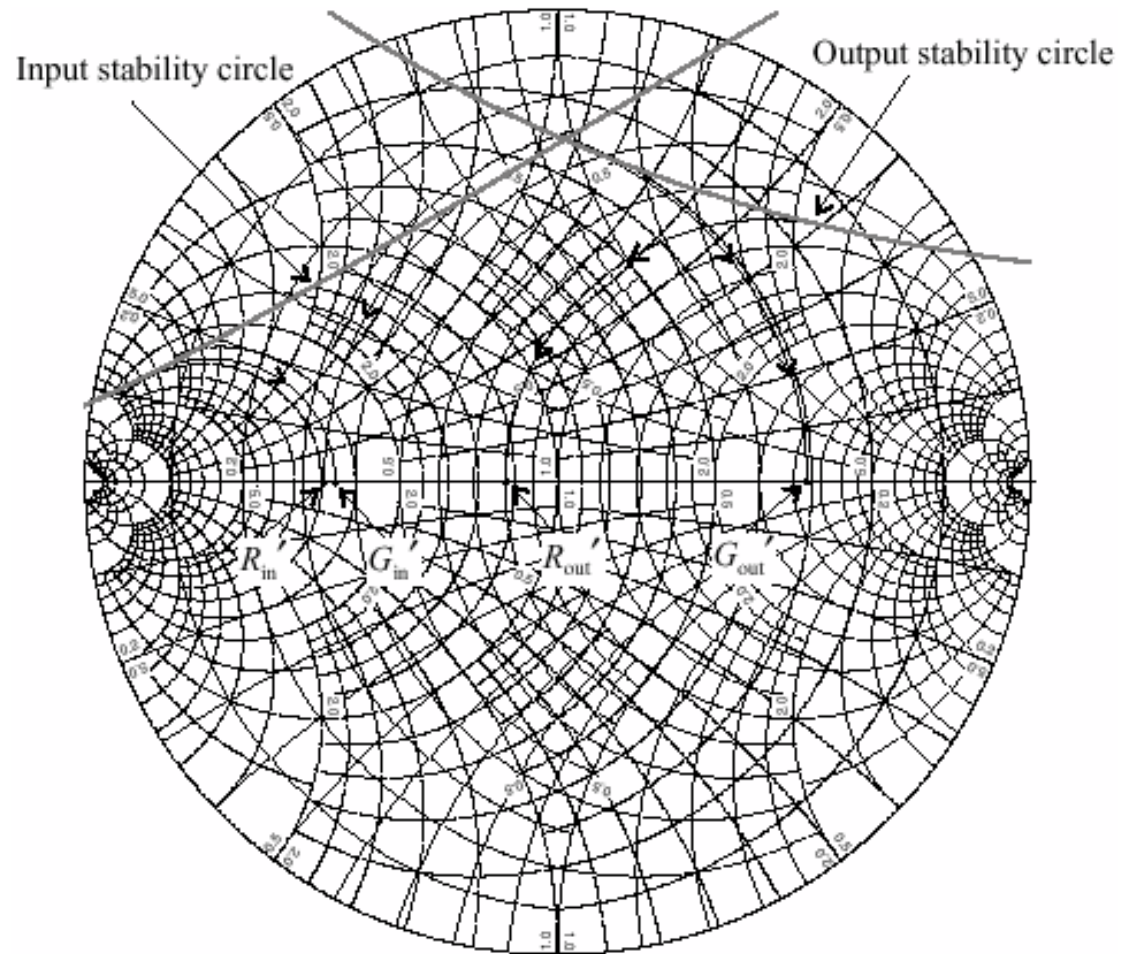
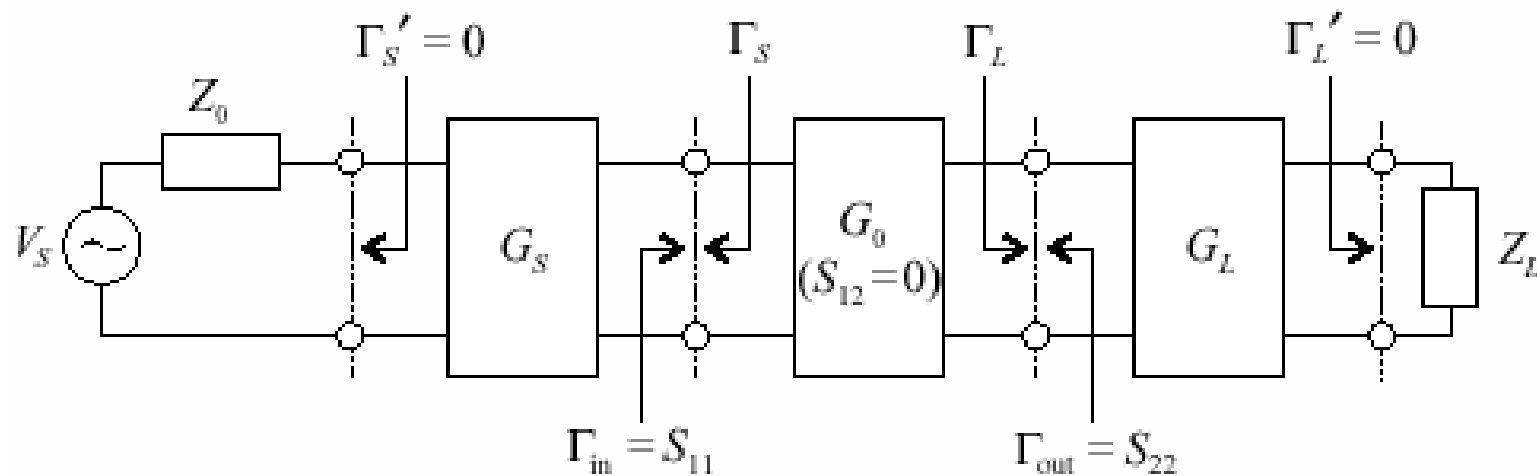
## Constant Gain: Unilateral Design ( $S_{12} = 0$ )

- Need to obtain desired gain performance
- Basically we can “detune” the amp matching networks for desired gain
- Unilateral power gain  $G_{TU}$  implies  $S_{12} = 0$



# Unilateral Power Gain Equations

- Unilateral Power gain

$$G_{TU} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} = G_S G_0 G_L$$

- Individual blocks are:

$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2}; \quad G_0 = |S_{21}|^2; \quad G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

- $G_{TU} \text{ (dB)} = G_S \text{ (dB)} + G_0 \text{ (dB)} + G_L \text{ (dB)}$



## Unilateral Gain Circles

- If  $|S_{11}| < 1$  and  $|S_{22}| < 1$  maximum unilateral power gain  $G_{TU\max}$  when  $\Gamma_S = S_{11}^*$  and  $\Gamma_L = S_{22}^*$

$$G_{S\max} = \frac{1}{1 - |S_{11}|^2}; \quad G_{L\max} = \frac{1}{1 - |S_{22}|^2}$$

- Normalized  $G_S$  w.r.t. maximum:

$$g_S = \frac{G_S}{G_{S\max}} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} (1 - |S_{11}|^2)$$

## Unilateral Gain Circles

- Normalized  $G_L$  w.r.t. maximums:

$$g_L = \frac{G_L}{G_{L\max}} = \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} (1 - |S_{22}|^2)$$

- Results in circles with center and radii:


$$d_{g_i} = \frac{g_i S_{ii}}{1 - |S_{ii}|^2 (1 - g_i)}; \quad r_{g_i} = \frac{\sqrt{1 - g_i} (1 - |S_{ii}|^2)}{1 - |S_{ii}|^2 (1 - g_i)}$$

$ii = 11$  or  $22$  depending on  $i = S$  or  $L$

## Gain Circle Observations

- $G_{i \max}$  when  $\Gamma_i = S_{ii}^*$  and  $d_{gi} = S_{ii}^*$  of radius  $r_{gi} = 0$
- Constant gain circles all have centers on line connecting the origin to  $S_{ii}^*$
- For the special case  $\Gamma_i = 0$  the normalized gain is:  
 $g_i = 1 - |S_{ii}|^2$  and  $d_{gi} = r_{gi} = |S_{ii}|/(1 + |S_{ii}|^2)$
- This implies that  $G_i = 1$  (0dB) circle always passes through origin of  $\Gamma_i$  - plane

# Input Matching Network Gain Circles

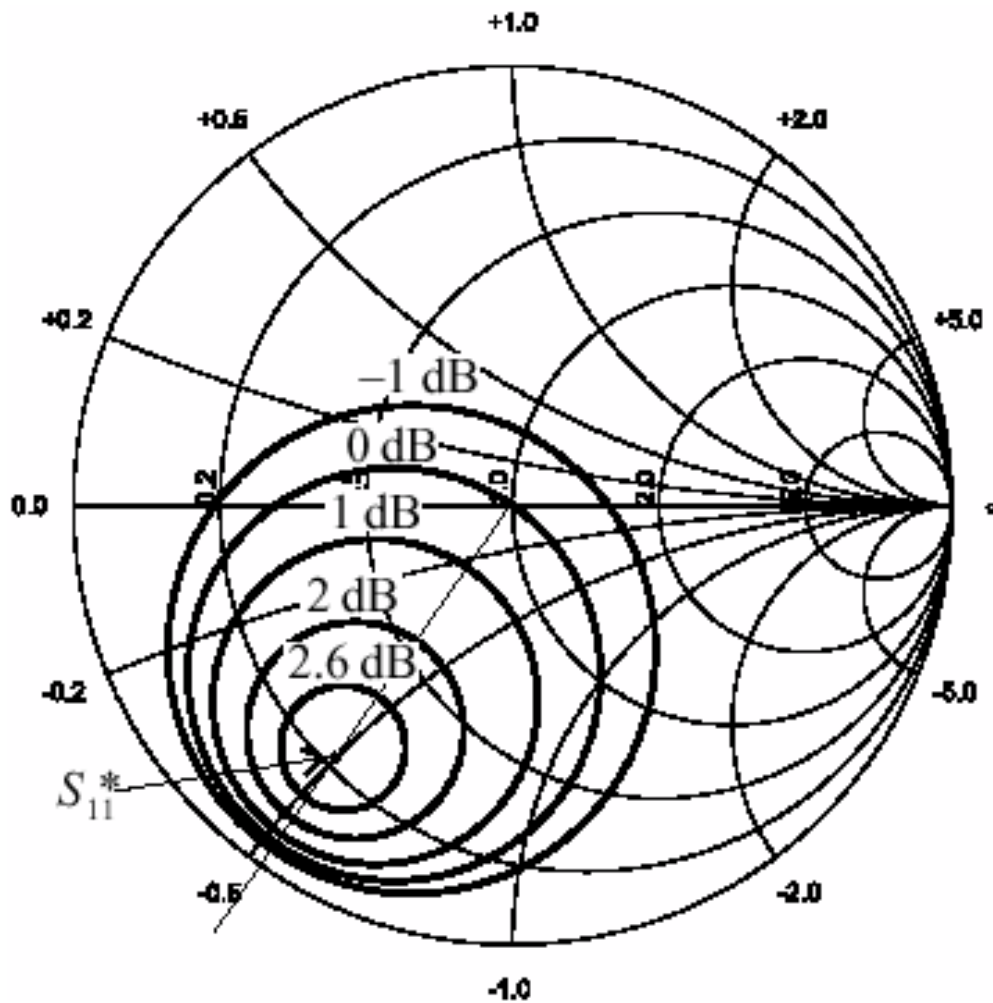

$\Gamma_S$  is detuned  
implying the  
matching  
network is  
detuned

## Bilateral Amplifier Design ( $S_{12}$ included)

- Complete equations required taking into account  $S_{12}$ : Thus  $\Gamma_S^* \neq S_{11}$  and  $\Gamma_L^* \neq S_{22}$

$$\Gamma_S^* = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = \frac{S_{11} - \Gamma_L\Delta}{1 - S_{22}\Gamma_L}$$

$$\Gamma_L^* = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} = \frac{S_{22} - \Gamma_S\Delta}{1 - S_{11}\Gamma_S}$$

# Bilateral Conjugate Match

- Matched source reflection coefficient

$$\Gamma_{MS} = \frac{B_1}{2C_1} - \frac{1}{2} \sqrt{\left(\frac{B_1}{C_1}\right)^2 - 4 \frac{C_1^*}{C_1}}$$

$$C_1 = S_{11} - S_{22}^* \Delta; \quad B_1 = 1 - |S_{22}|^2 - |\Delta|^2 + |S_{11}|^2$$

- Matched load reflection coefficient

$$\Gamma_{ML} = \frac{B_2}{2C_2} - \frac{1}{2} \sqrt{\left(\frac{B_2}{C_2}\right)^2 - 4 \frac{C_2^*}{C_2}}$$

$$C_2 = S_{22} - S_{11}^* \Delta; \quad B_2 = 1 - |S_{11}|^2 - |\Delta|^2 + |S_{22}|^2$$

# Optimum Bilateral Matching

$$\Gamma_{MS}^* = S_{11} + \frac{S_{12}S_{21}\Gamma_{ML}}{1 - S_{22}\Gamma_{ML}}$$

$$\Gamma_{ML}^* = S_{22} + \frac{S_{12}S_{21}\Gamma_{MS}}{1 - S_{11}\Gamma_{MS}}$$

## Design Procedure for RF BJT Amps

- Bias the circuit as specified by data sheet with available S-Parameters
- Determine S-Parameters at bias conditions and operating frequency
- Calculate stability  $|k| > 1$  and  $|\Delta| < 1$ ?
- If unconditionally stable, design for gain
- If  $|k| \leq 1$  and  $|\Delta| \geq 1$  then draw Stability Circles on Smith Chart by finding  $r_{out}$ ,  $C_{out}$ ,  $r_{in}$ , and  $C_{in}$  radii and distances for the circles



## Design Procedure for RF BJT Amps


- Determine if  $\Gamma_L$  ( $S_{22}^*$  for conjugate match) lies in unstable region – do same for  $\Gamma_S$
- If stable, no worries.
- If unstable, add small shunt or series resistance to move effective  $S_{22}^*$  into stable region – use max outer edge real part of circle as resistance or conductance (do same for input side)
- Can adjust gain by detuning  $\Gamma_L$  or  $\Gamma_S$

# Design Procedure for RF BJT Amps


- To design for specified gain, must be less than  $G_{TU \max}$  (max unilateral gain small  $S_{12}$ )
- Recall that (know  $G_0 = |S_{21}|^2$ )  
$$G_{TU} [\text{dB}] = G_S [\text{dB}] + G_0 [\text{dB}] + G_L [\text{dB}]$$
- Detune either  $\Gamma_S$  or  $\Gamma_L$
- Draw gain circles for  $G_S$  (or  $G_L$ ) for detuned  $\Gamma_S$  (or  $\Gamma_L$ ) matching network
- Overall gain is reduced when designed for (a) Stability and (b) detuned matching network
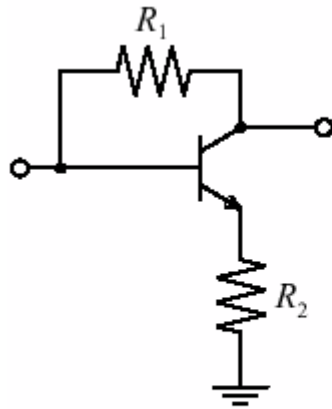
# Design Procedure for RF BJT Amps

- Further circles on the Smith Chart include noise circles and constant VSWR circles
- Broadband amps often are feedback amps




(a) Feedback in BJTs

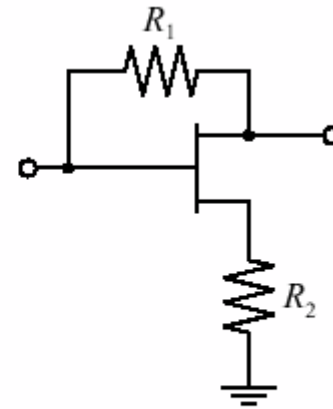


(b) Feedback in FETs

# RF Shunt-Shunt Feedback Amp Design

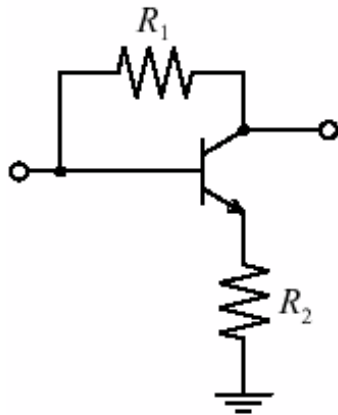

(a) Feedback in BJTs

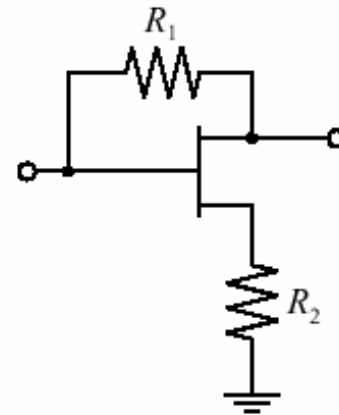


(b) Feedback in FETs

$$R_1 = Z_0 (1 - S_{21}) \quad R_2 = \frac{Z_0^2}{R_1} - \frac{1}{g_m}$$


$$g_m = \frac{I_C}{V_T}$$

$S_{21}$  calculated from desired gain  $G$

# Distortion: 1 dB Compression

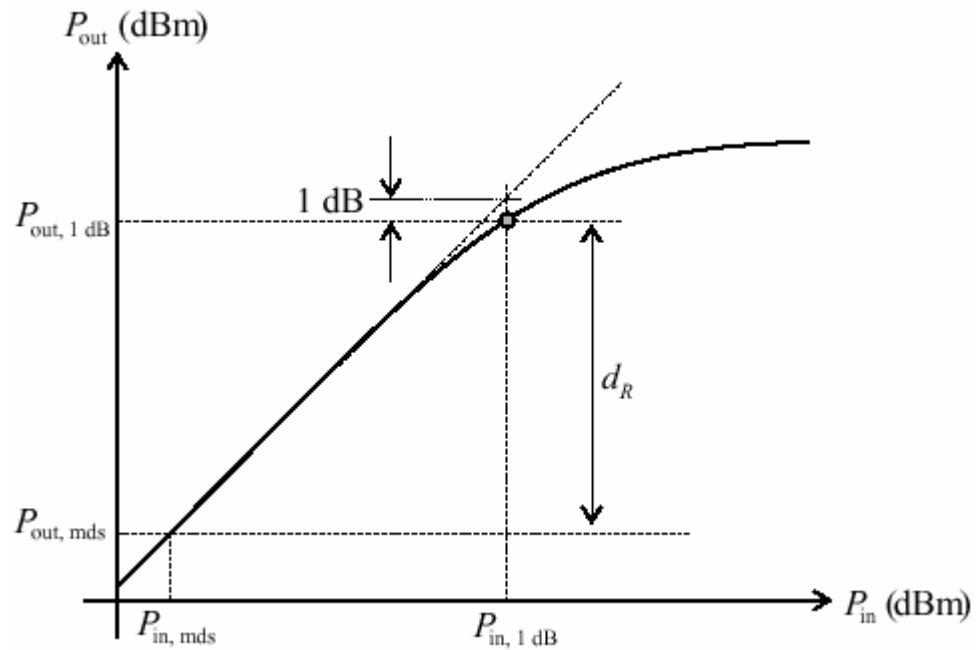

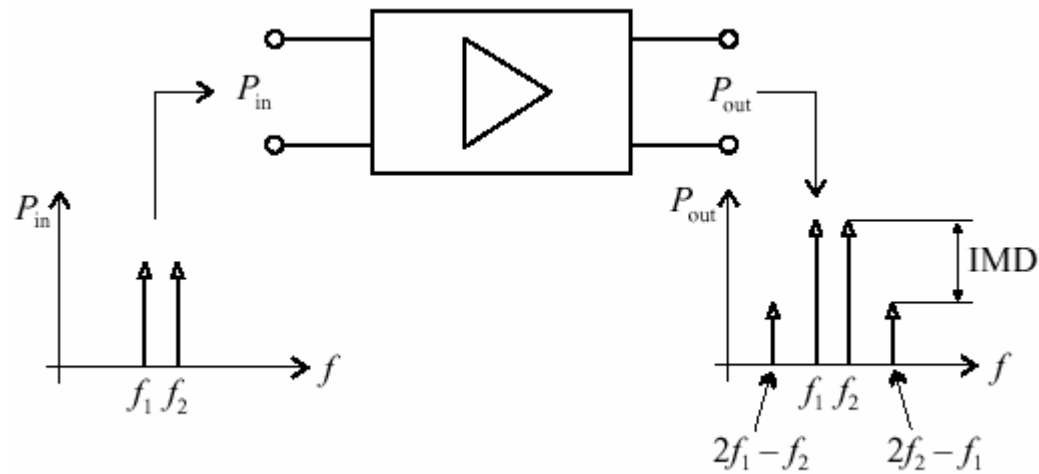
# Distortion: 3<sup>rd</sup> Order Intermodulation Distortion


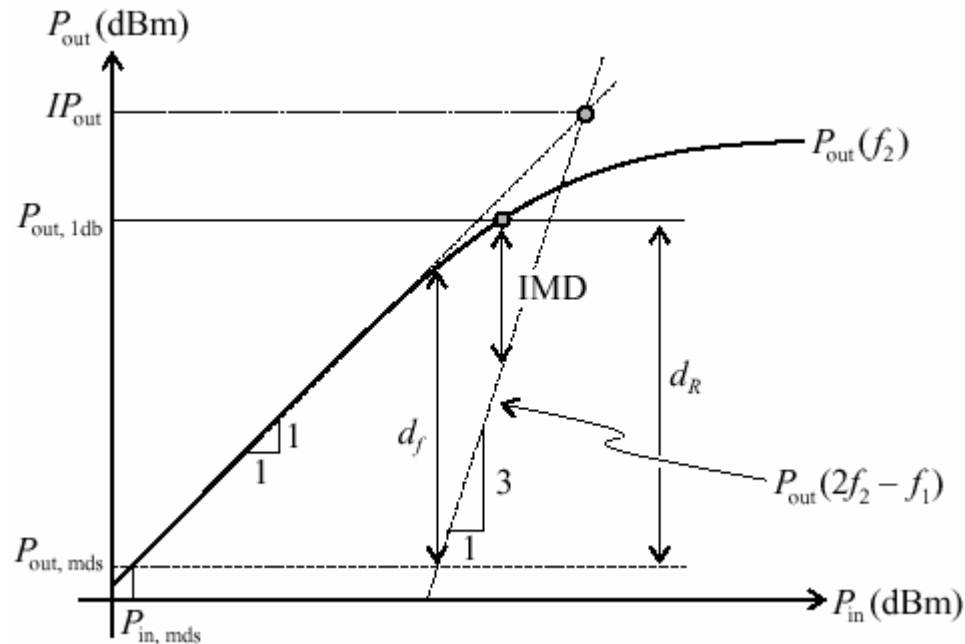
# Distortion: 3<sup>rd</sup> Order IMD

$$IMD3[\text{dB}] = P_{out}(f_2)[\text{dBm}] - P_{out}(2f_2 - f_1)[\text{dBm}]$$



$$d_f [\text{dB}] = \frac{2}{3} (IP [\text{dBm}] - G_0 [\text{dB}] - P_{in, mds} [\text{dBm}])$$

Spurious Free Dynamic Range